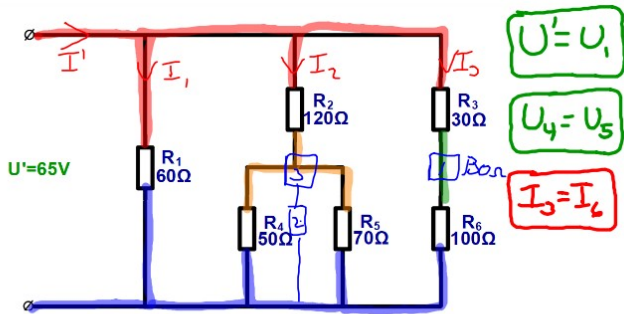




	U	I	R
1	65	1,08 A	60Ω
2	52,29 V	435,75 mA	120Ω
3	15 V	500 mA	30Ω
4	12,71 V	254,19 mA	50Ω
5	12,71 V	181,56 mA	70Ω
6	50 V	500 mA	100Ω
Total	65 V	2,02 A	32,19Ω

$$(12) U_4 = U' - U_2 = \underline{12,71 V}$$

$$(13) I_4 = \frac{U_4}{R_4} = 254,19 \text{ mA}$$

$$(14) I_5 = \frac{U_5}{R_5} / I_5 = I_2 - I_4 = 181,56 \text{ mA}$$

$$(1) R_{3,6} = R_3 + R_6 = \underline{130 \Omega}$$

$$(2) R_{4,5} = (R_4^{-1} + R_5^{-1})^{-1} = \underline{29,17 \Omega}$$

$$(3) R_{2,4,5} = R_2 + R_{4,5} = \underline{149,17 \Omega}$$

$$(4) R' = (R_1^{-1} + R_{2,4,5}^{-1} + R_{3,6}^{-1})^{-1} = \underline{32,19 \Omega}$$

$$(5) I' = \frac{U'}{R'} = \underline{2,02 A}$$

$$(6) I_1 = \frac{U_1}{R_1} = \underline{1,08 A}$$

$$(7) I_3 = \frac{U'}{R_{3,6}} = \underline{500 \text{ mA}}$$

$$(8) I_2 = I' - I_1 - I_3 = \underline{435,75 \text{ mA}}$$

$$(9) U_2 = I_2 \times R_2 = \underline{52,29 V}$$

$$(10) U_3 = I_3 \times R_3 = \underline{15 V}$$

$$(11) U_6 = I_3 \times R_6 / U_6 = U' - U_3 = \underline{50 V}$$