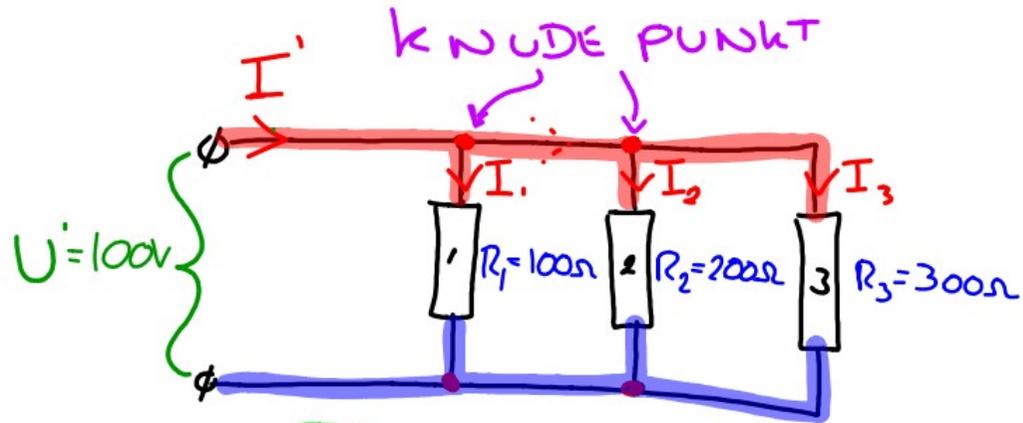


PARALLEL KREDS



$$U' = U_1 = U_2 = U_3$$

	U	I	R
1	100V	1 A	100Ω
2	100V	500mA	200Ω
3	100V	333,33mA	300Ω
Tot	100V	1,83A	54,55Ω

$$I_1 = \frac{U_1}{R_1} = \frac{100}{100} = \underline{1A}$$

$$I_2 = \frac{U_2}{R_2} = \frac{100}{200} = \underline{500mA}$$

$$I_3 = \frac{U_3}{R_3} = \frac{100}{300} = \underline{333,33mA}$$


$$I' = I_1 + I_2 + I_3 = 1 + 0,5 + 0,33333 = \underline{1,83A}$$

$$R' = \frac{U'}{I'} = \frac{100}{1,83} = \underline{54,55\Omega}$$

$$R' = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \Rightarrow R' = (R_1^{-1} + R_2^{-1} + R_3^{-1})^{-1}$$

DEN REC' BROKKE REGNE METODE

$$U' = 12V$$

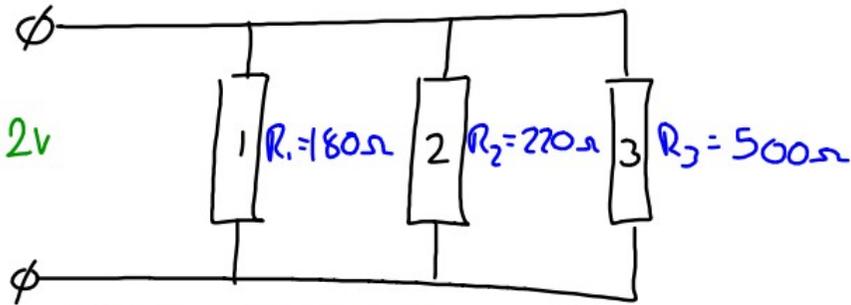

$$U' = U_1 = U_2 = U_3$$

	U	I	R
1	↑		180Ω
2			220Ω
3			500Ω
Tot	12V		82,64Ω

$$I_1 = \frac{U_1}{R_1} =$$


$$I_2 = \frac{U_2}{R_2} =$$

$$I_3 = \frac{U_3}{R_3} =$$


$$I' = I_1 + I_2 + I_3 =$$

$$R' = \frac{U'}{I'} =$$
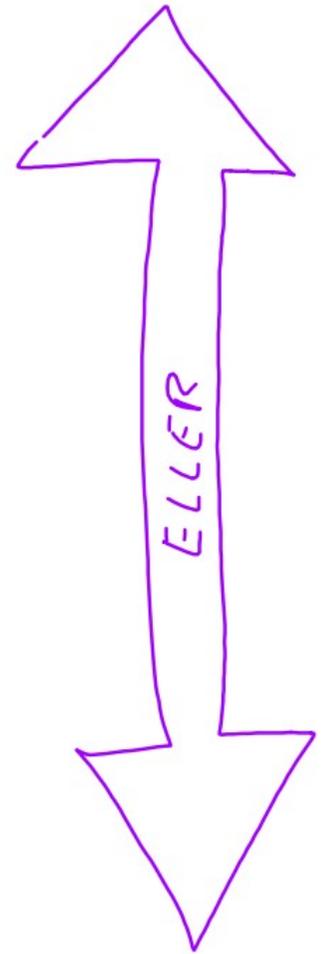
$$R' = (R_1^{-1} + R_2^{-1} + R_3^{-1})^{-1} =$$



TAVLE OPGAVE

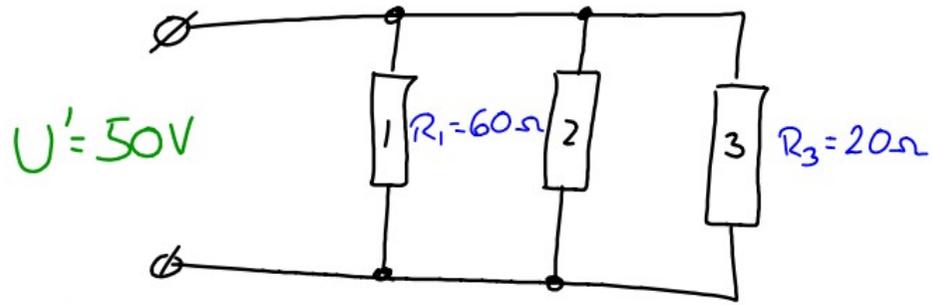

$U' = 50V$

$R' = 11.5\Omega$

$U' = U_1 = U_2 = U_3$

	U	I	R
1	↑	833.33mA	60Ω
2		1.04A	49.29Ω
3		2.5A	20Ω
Tot		50V	4.35A

① $I' = \frac{U'}{R'} = \frac{50}{11.5} = \underline{\underline{4.35A}}$

② $I_1 = \frac{U_1}{R_1} = \frac{50}{60} = \underline{\underline{833.33mA}}$


③ $I_3 = \frac{U_3}{R_3} = \frac{50}{20} = \underline{\underline{2.5A}}$

④ $I_2 = I' - I_1 - I_3 = 4.35 - 0.83 - 2.5 = \underline{\underline{1.01A}}$

⑤ $R_2 = \frac{U_2}{I_2} = \frac{50}{1.01} = \underline{\underline{49.29\Omega}}$

⑥ $R' = (R_1^{-1} + R_2^{-1} + R_3^{-1})^{-1} = (60^{-1} + 49.29^{-1} + 20^{-1})^{-1} = \underline{\underline{11.5\Omega}}$

TAVLE OPGAVE

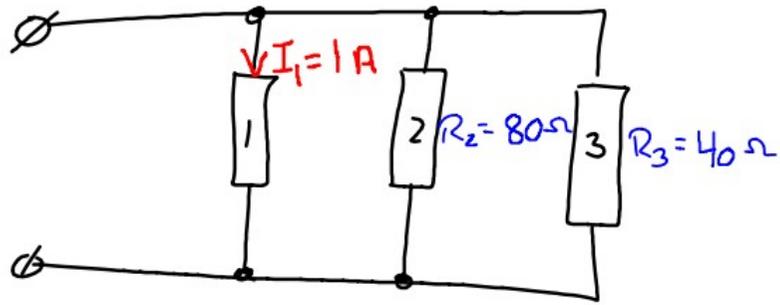

$$R' = 12,9 \Omega$$

$$U' = U_1 = U_2 = U_3$$


	U	I	R
1	24,99V	1 A	24,99Ω
2	- -		80Ω
3	- -		40Ω
Tot	- -		12,9Ω

SERIE

$$R' = R_1 + R_2 + R_3$$
$$R_1 = R' - R_2 - R_3$$

$$R' = (R_1^{-1} + R_2^{-1} + R_3^{-1})^{-1}$$
$$R_1 = (R'^{-1} - R_2^{-1} - R_3^{-1})^{-1}$$



GULD KORN / COWBOY TRICK

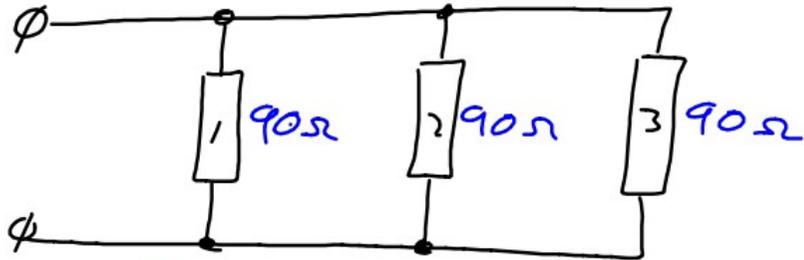

$$R' = (R_1^{-1} + R_2^{-1} + R_3^{-1})^{-1}$$

VED ENS STØRRELS \rightarrow
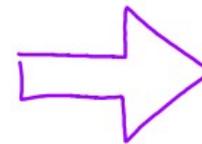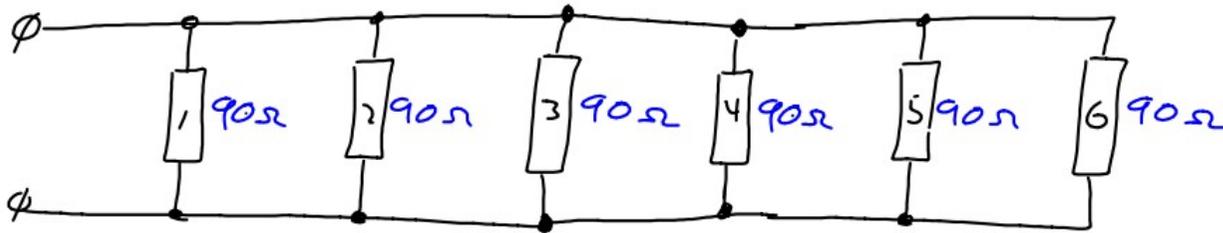
$$\frac{R_x}{\text{ANTAL}} \quad R' = \frac{90}{3} = \underline{\underline{30\Omega}}$$



$$R' = \frac{90}{6} = \underline{\underline{15\Omega}}$$