

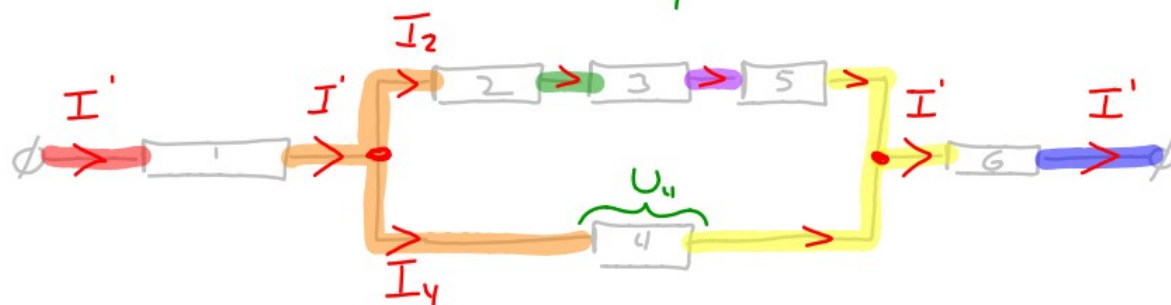
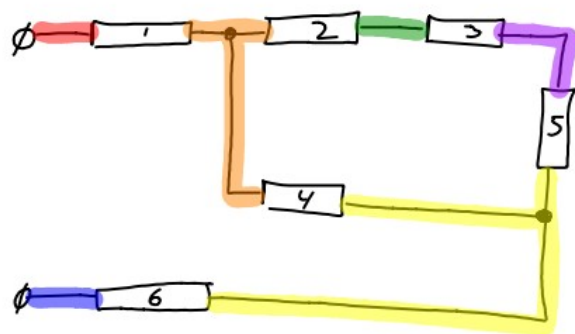
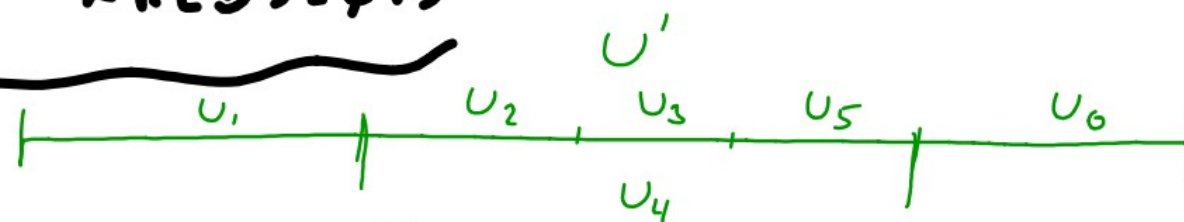


OMTEGNING AF KREDSLØB

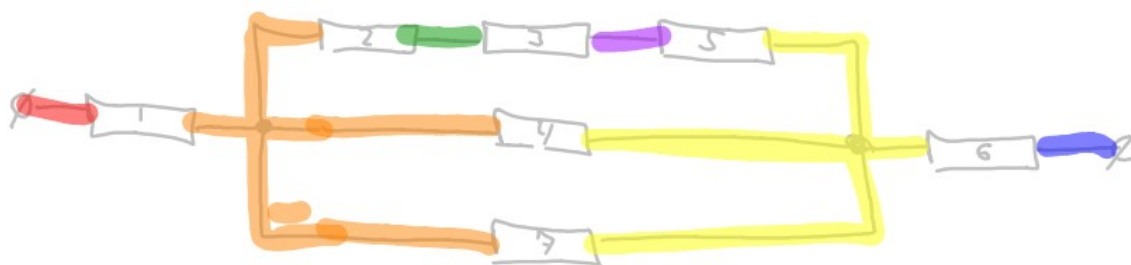

$$I' = I_1 = I_6$$

$$I_2 = I_3 = I_5$$

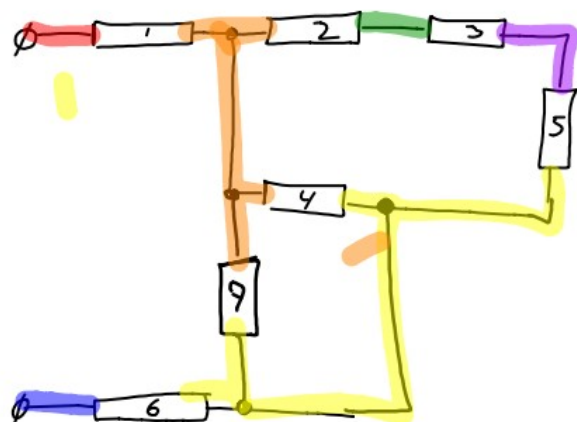

$$I' = I_1 = I_6$$

$$I_2 = I_3 = I_5$$

$$U_4 = U_7$$